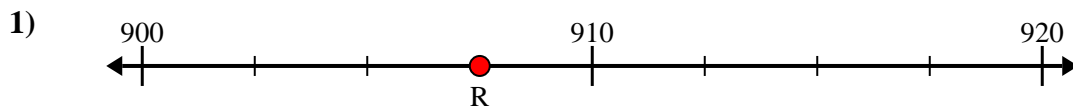





Find the value of R.


Answers



1. _____

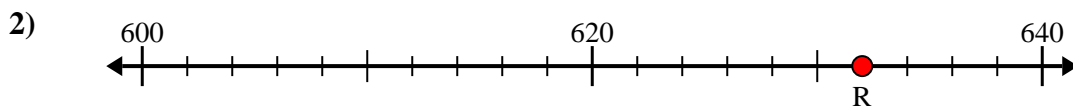


2. _____

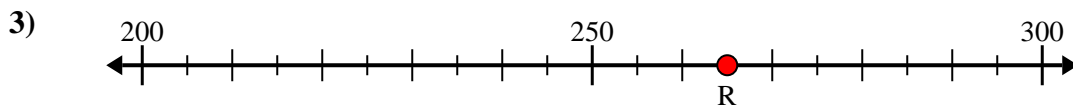


3. _____

4. _____

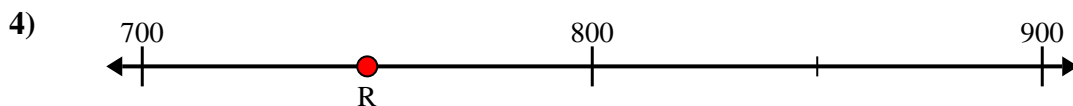


5. _____

6. _____

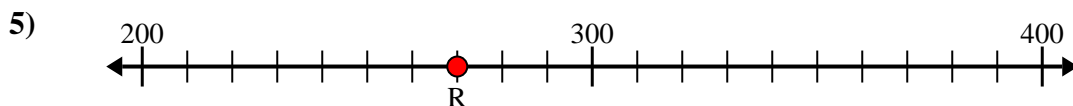





7. _____

8. _____

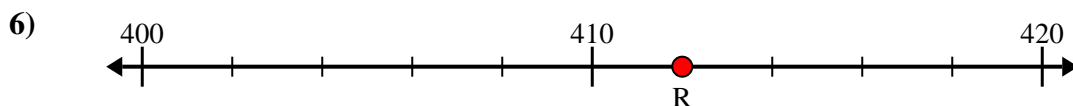











9. _____

10. _____

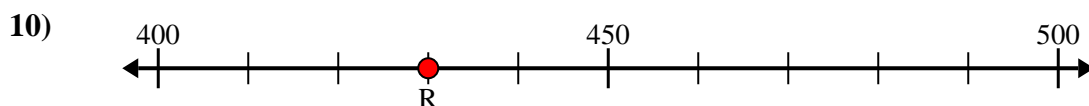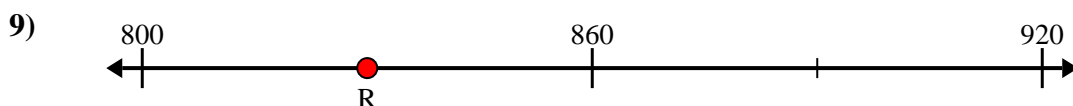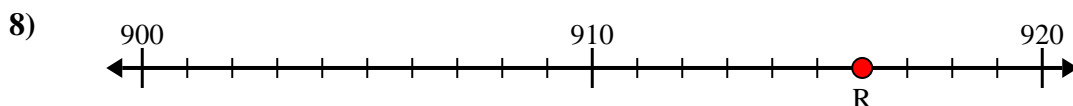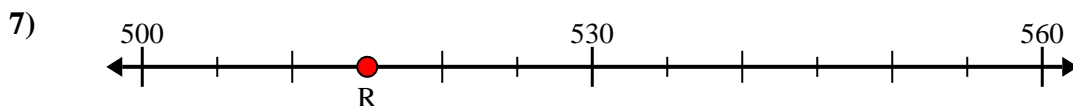



Find the value of R.

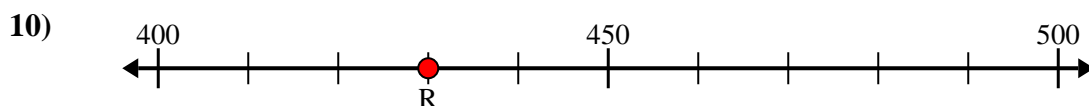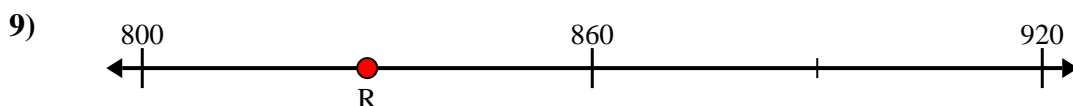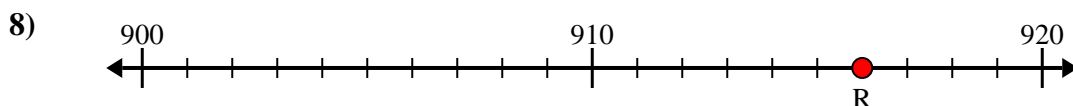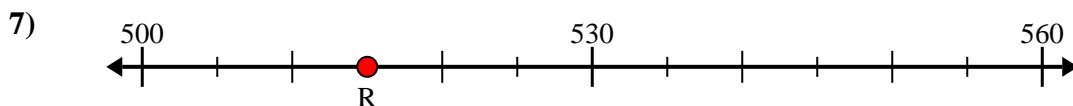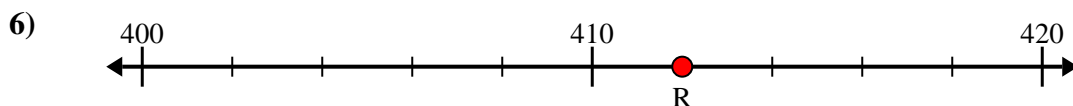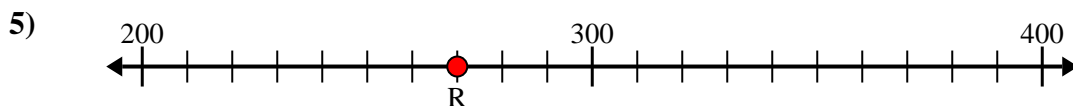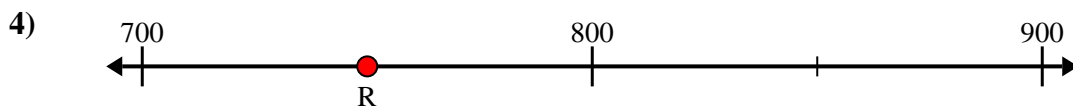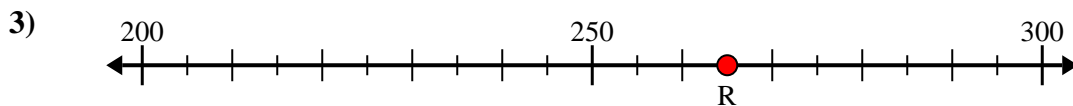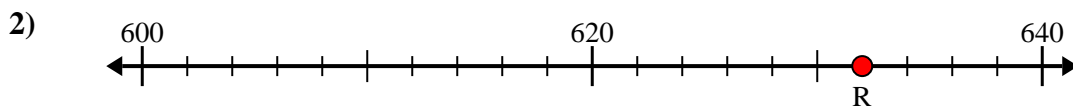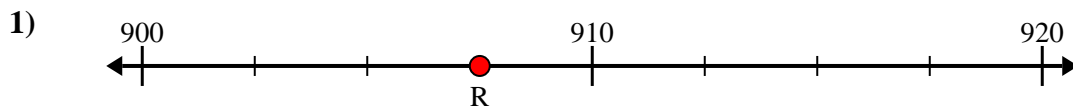

Answers

1. 907.5

2. 632

3. 265

4. 750

5. 270

6. 412

7. 515

8. 916

9. 830

10. 430