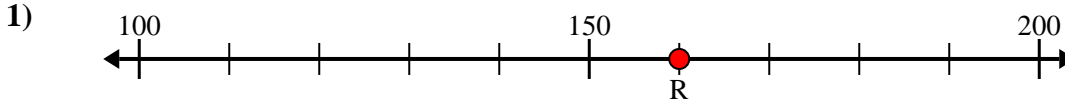





Find the value of R.


Answers




1. _____

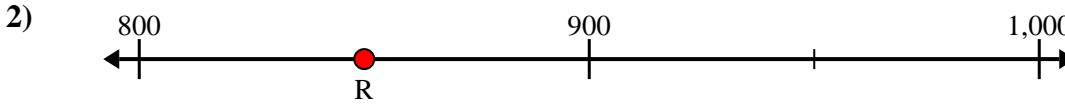


2. _____

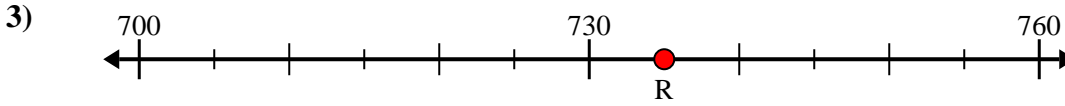


3. _____

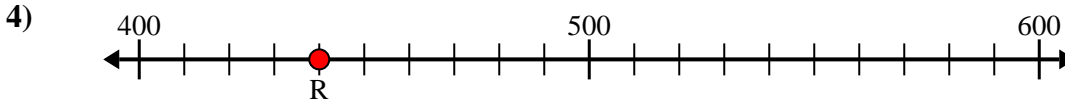


4. _____

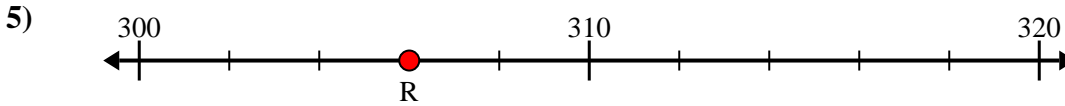


5. _____

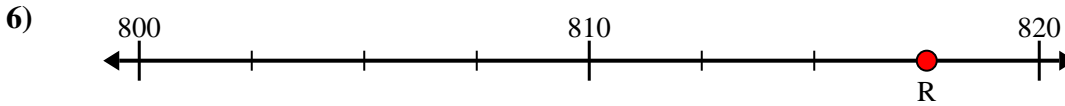


6. _____

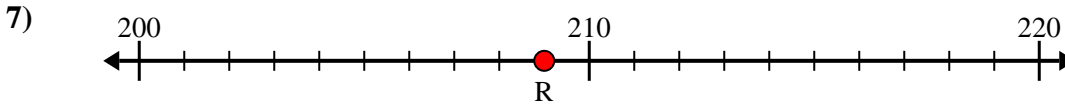


7. _____

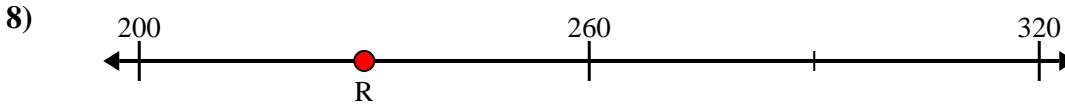

8. _____

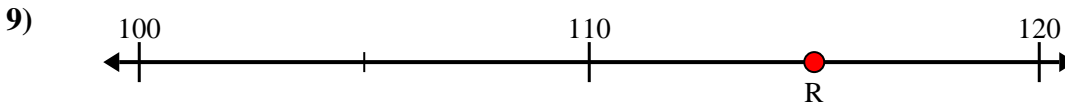











9. _____

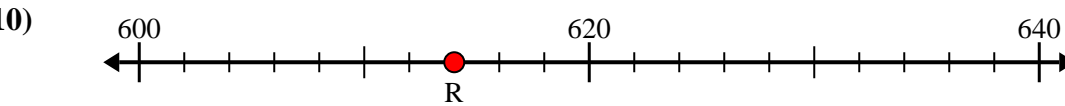

10. _____



Find the value of R.

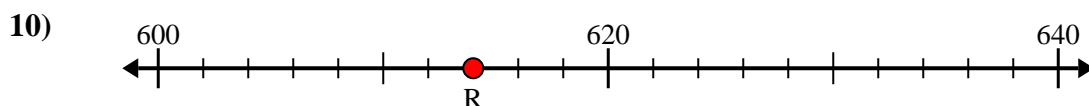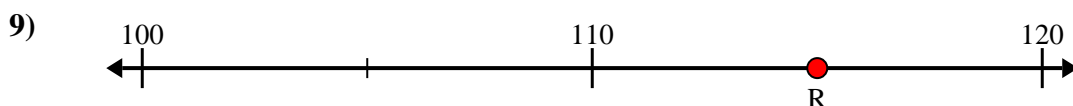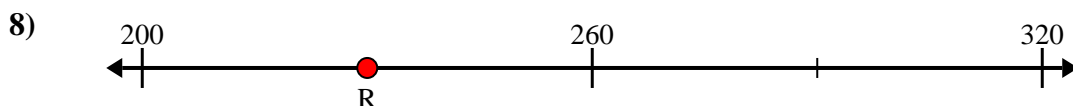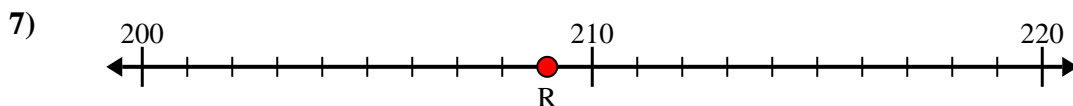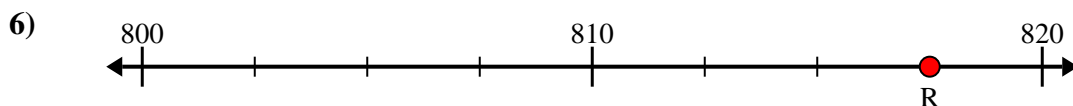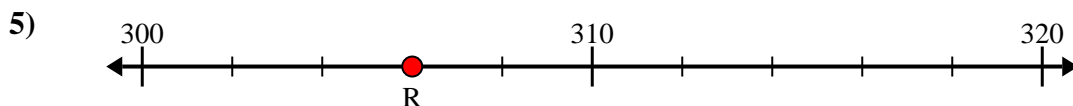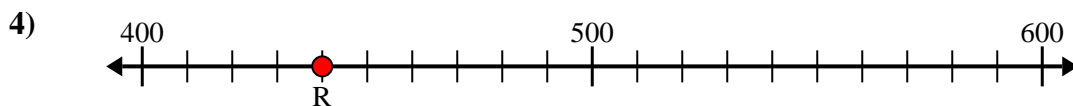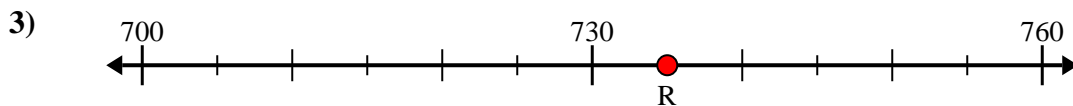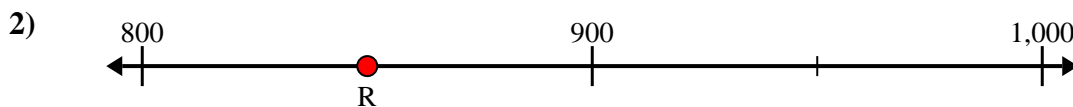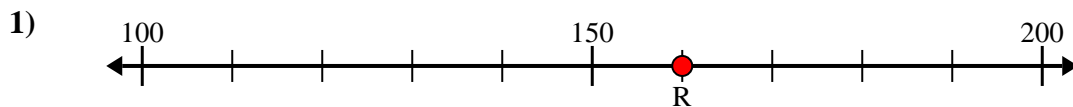

Answers

1. 160

2. 850

3. 735

4. 440

5. 306

6. 817.5

7. 209

8. 230

9. 115

10. 614